

## Digital Frequency Multiplier


A digital electronics circuit that multiplies an input frequency by 64.

### Input Signal Characteristics

- 3.3V peak to peak digital waveform
- Minimum duty cycle of 5%
- Minimum frequency 23.4375 KHz
- Maximum frequency 78.125 KHz

### Output Signal Characteristics

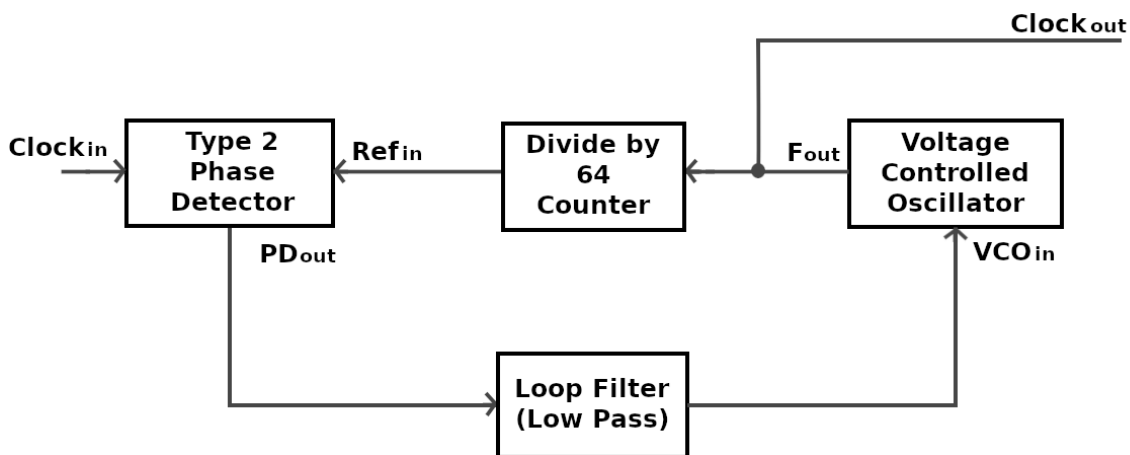- 3.3V peak to peak digital waveform
- Duty cycle of 50%
- Minimum frequency 1.5 MHz
- Maximum frequency 5.0 MHz



### Phased Lock Loop as Frequency Synthesizer

#### Using a Phase Locked Loop as a Frequency Synthesizer

A simplified explanation of the operation of a phase locked loop (PLL) is as follows:  
There are three main components:

- Phase Detector (in this case type 2)
- Loop Filter
- Voltage Controlled Oscillator (VCO)

The phase detector compares two input signals, **Clock<sub>in</sub>** and **Ref<sub>in</sub>**. The difference in phase between the signals is output as a series of pulses, **PD<sub>out</sub>**.

A type 2 phase detector outputs 'positive' pulses when the phase of **Clock<sub>in</sub>** leads that of **Ref<sub>in</sub>** and 'negative' pulses when it lags that of **Ref<sub>in</sub>**.

The pulses are converted into a DC voltage by the loop filter, which acts as a low pass filter (integrator). The greater the phase difference, the higher the DC voltage.


The loop filter's output is the control input voltage to the VCO.

The VCO outputs a frequency that is proportional to the input voltage, the higher the voltage, the greater the frequency.

(1nF and 100nF decoupling capacitors were placed close to the power supply pins of U3).
 
## Prototype


The prototype board contains 3 frequency multipliers and was used in the PTP instrumentation control project




Prototype Hardware

## Results

Shown below are the oscilloscope traces for clock in, phase detector output and clock out.

 


Clock In – 62.50KHz

 

Phase Detector Output

 Note the 'positive' and 'negative' pulses. This is a characteristic of a type 2 phase detector. The pulses are very narrow because Clock in and Ref in are almost in phase.



Clock Out – 4MHz

### Conclusions

An accurate multiplication of an input signal's frequency was possible, producing an output signal with a 50% duty cycle.